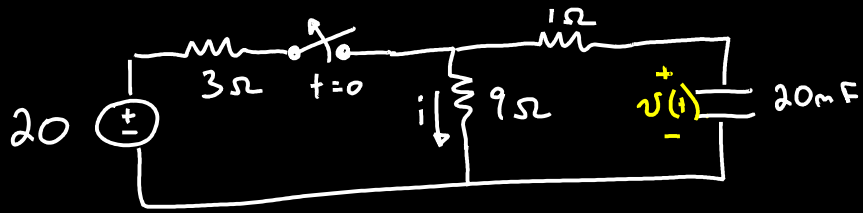


# First Order Problem



Find  $i$  for all time

①  $V_o = v_c(t=0) : t < 0 = \boxed{15V}$


②  $\tau$

③  $V_\infty$


④  $v(t) = V_\infty + (V_o - V_\infty) e^{-t/\tau}$

⑤  $i(t)$

⑥ All time

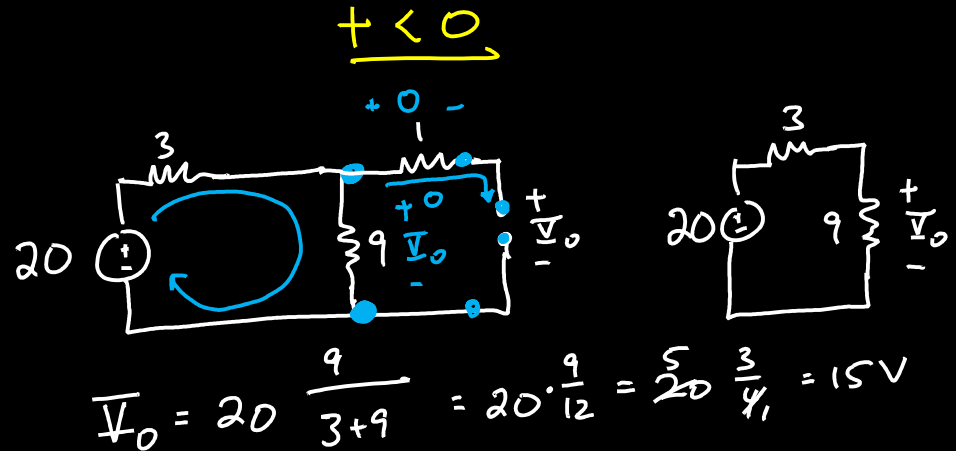

# First Order Problem

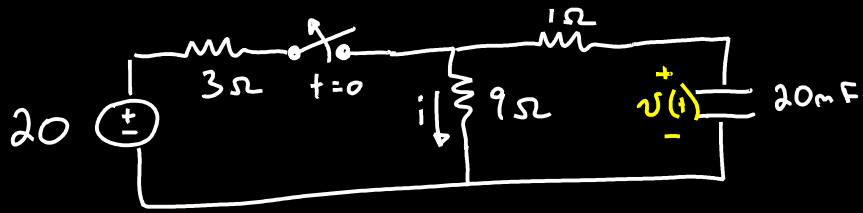

Find  $i$  for all time

①  $V_o = v_c(t \leq 0) : t < 0 = \boxed{15V}$


②  $\tau : 0 < t < \infty = \boxed{\frac{1}{5} s}$

③  $V_\infty$

④  $v(t) = V_\infty + (V_o - V_\infty) e^{-t/\tau}$

⑤  $i(t)$

⑥ All time

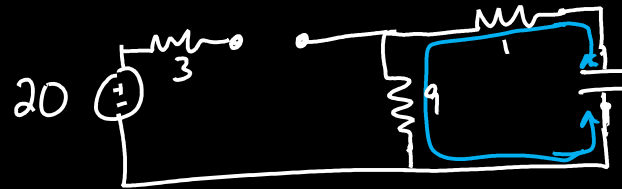


$R_{eq} = 1 + 9 = 10 \Omega$

$C = 20mF$

$\tau = RC$   
 $= (10)(20m)$

$= 200m$   
 $= \boxed{\frac{1}{5} s}$

# First Order Problem

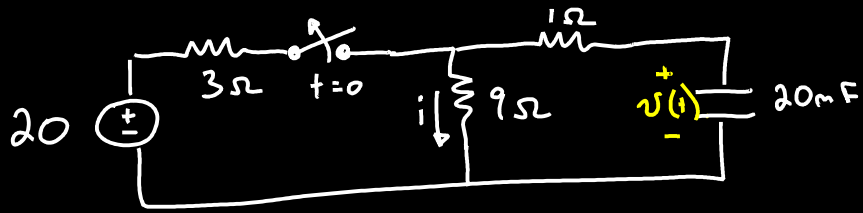

Find  $i$  for all time

①  $V_o = v_c(t=0) : t < 0 = \boxed{15V}$


②  $\tau : 0 < t < \infty = \boxed{\frac{1}{5} s}$

③  $V_\infty = v_c(t=\infty) : t = \infty = \boxed{0V}$

④  $v(t) = V_\infty + (V_o - V_\infty) e^{-t/\tau}$


⑤  $i(t)$

⑥ All time

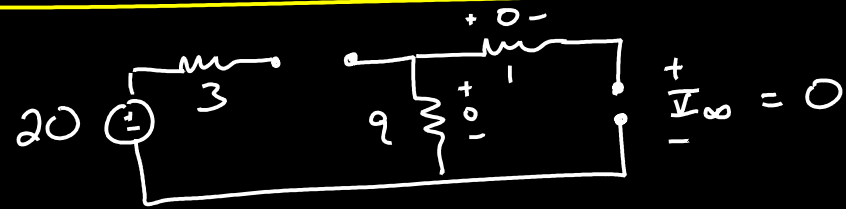

no switches  
no cap, inductors  
no  $v(t)$

# First Order Problem

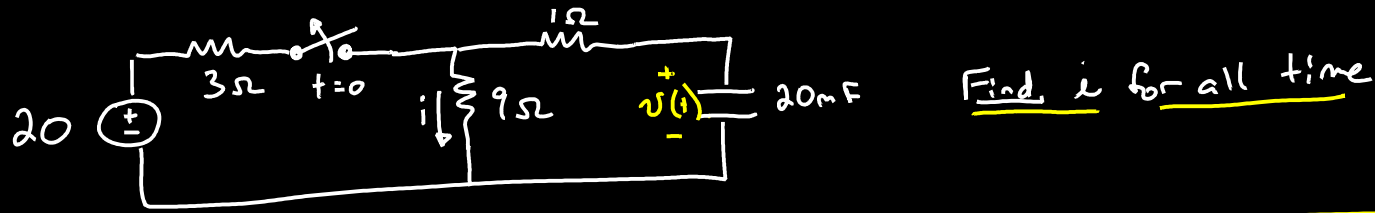

①  $V_o = v_c(t=0) : t < 0 = \boxed{15V}$

②  $\tau : 0 < t < \infty = \boxed{\frac{1}{5} s}$

③  $V_\infty = v_c(t=\infty) : t = \infty = \boxed{0V}$

④  $v_c(t) = V_\infty + (V_o - V_\infty) e^{-t/\tau} = \begin{cases} 15, & t < 0 \\ \boxed{15e^{-5t} V}, & t \geq 0 \end{cases}$

⑤  $i(t) = \begin{cases} \frac{20}{3} A, & t < 0 \\ \boxed{1.5e^{-5t} A}, & t \geq 0 \end{cases}$

⑥ All time

$t > 0$

$$i(t) = \frac{v(t)}{R} = \frac{15e^{-5t}}{10} = \boxed{1.5e^{-5t} A}$$

$t < 0$

$$i = \frac{20}{3+9} = \frac{20}{12} = \frac{5}{3}$$