

$$\left. \begin{aligned} i &= C v' \\ v &= \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0) \\ v &= L i' \\ i &= \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0) \end{aligned} \right\} \begin{array}{l} \text{Cap} \\ \text{Ind} \end{array}$$

$$i(t) = \begin{cases} t^2, & 0 < t \leq 1 \\ 1, & 1 < t \leq 2 \\ -1(t-3), & 2 < t \leq 3 \\ 0, & t > 3 \end{cases}$$

Find $v(t)$ if $v(t=0)=0$, $t > 0$

time regions	t_0	$v(t_0)$	$i(t)$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$
$0 < t \leq 1$	0	0	t^2	$\frac{1}{12} \int_0^t \tau^2 d\tau + 0 = \frac{1}{12} \cdot \frac{1}{3} \tau^3 \Big _{\tau=0}^t + 0 = \frac{1}{36} t^3 = 4t^3 V$
$1 < t \leq 2$	1	$4 \cdot 1^3 = 4$	1	$\frac{1}{12} \int_1^t 1 d\tau + 4 = \frac{1}{12} \tau \Big _{\tau=1}^t + 4 = \frac{1}{12}(t-1) + 4 = 12t - 8 V$
$2 < t \leq 3$	2	$12 \cdot 2 - 8 = 16$	$3-t$	$\frac{1}{12} \int_2^t (3-\tau) d\tau + 16 = \frac{1}{12} \cdot \left[3\tau - \frac{1}{2}\tau^2 \right]_{\tau=2}^t + 16 = \frac{1}{12} \left[3t - \frac{1}{2}t^2 - \left(3 \cdot 2 - \frac{1}{2} \cdot 4 \right) \right] + 16 = \frac{1}{12} \left[3t - \frac{1}{2}t^2 - 4 \right] + 16 = 36t - 6t^2 - 32$
$t > 3$	3	$36 \cdot 3 - 6 \cdot 9 - 32 = 22$	0	$\frac{1}{12} \int_3^t 0 d\tau + 22 = 22$

$$v(t) = \begin{cases} 4t^3 V, & 0 < t \leq 1 \\ 12t - 8, & 1 < t \leq 2 \\ 36t - 6t^2 - 32, & 2 < t \leq 3 \\ 22, & t > 3 \end{cases}$$

Find $w(2)$

$$w_C(t) = \frac{1}{2} C v^2$$

$$w_L = \frac{1}{2} L i^2$$


$$= \frac{1}{2} \cdot C \cdot v^2(2)$$

$$= \frac{1}{2} \left(\frac{1}{12} \right) 16^2$$


$$= \frac{16^2}{24} = 10.7 J$$

$$v^2(2) = 12(2) - 8 = 16$$



2 DC Steady State

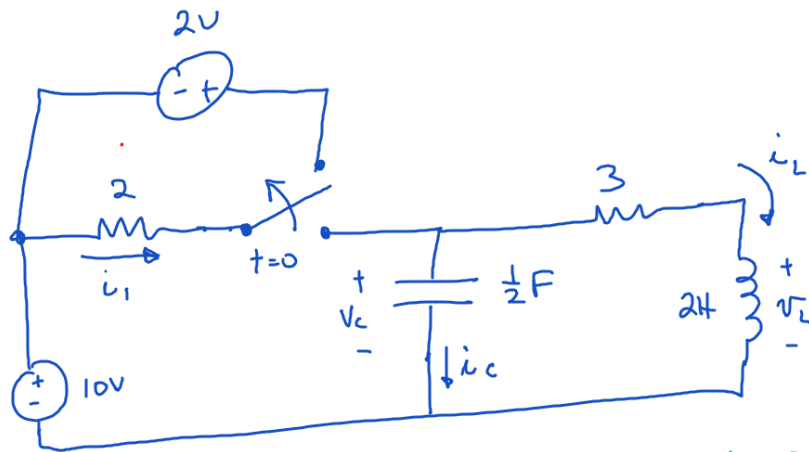

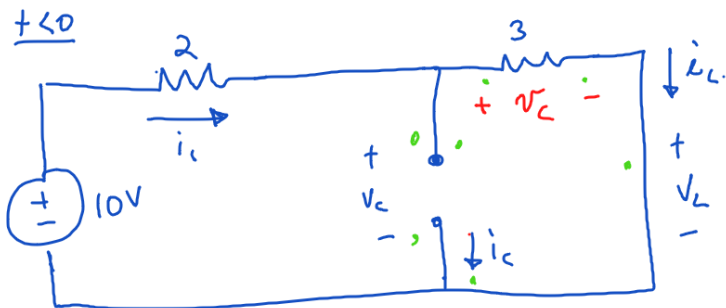a) Find i_1, i_c, i_L, v_C, v_L at both $t = -3$ and $t = 0^-$



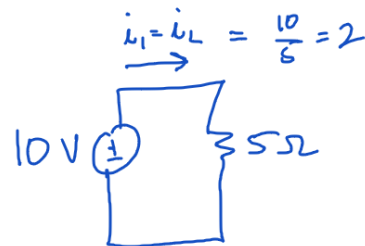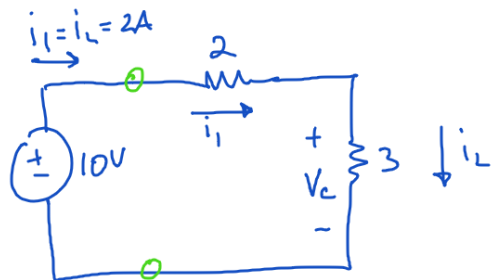
$$\begin{aligned} i_1 &= 2A \\ i_c &= 0A \\ i_L &= 2A \\ v_C &= (2A)(3\Omega) = 6V \\ v_L &= 0V \end{aligned}$$



Problem 2/5

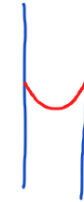b) Find $Q_c(t = -2)$

$$\begin{aligned} Q_c &= C \cdot V \\ &= \left(\frac{1}{2}\right)(6) \\ &= \boxed{3C} \end{aligned}$$




c) Find $W_L(t = 0^+)$

$$\begin{aligned} W_L &= \frac{1}{2} L i_L^2 \\ W_L(0^+) &= \frac{1}{2} (2) i_L^2(0^+) \\ &= \frac{1}{2} (2) i_L^2(0^-) \\ &= \frac{1}{2} (2) \cdot 2^2 \\ &= \boxed{4J} \end{aligned}$$

Voltage continuity for a cap
Voltage across a cap cannot change instantaneously

Current continuity for inductor
Current through an inductor cannot change inst.

3)


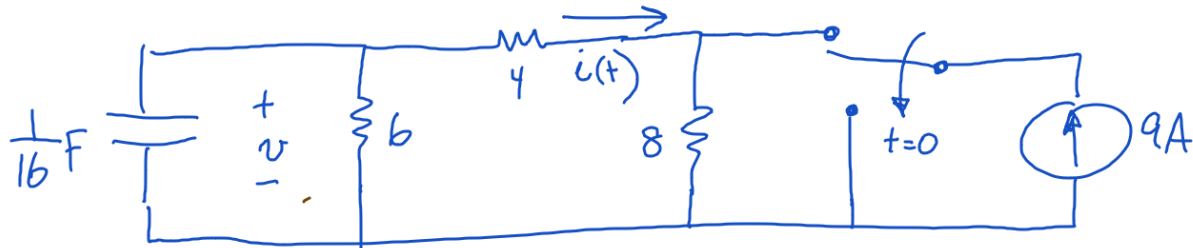


Voltage Dividers
Current Dividers

Problem 3/5

Find $v(t)$ and $i(t)$ for all time

① $t < 0$ V_{co}

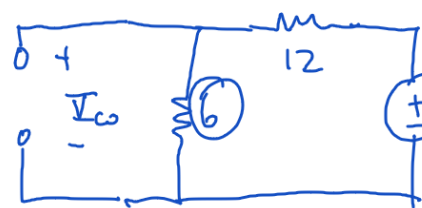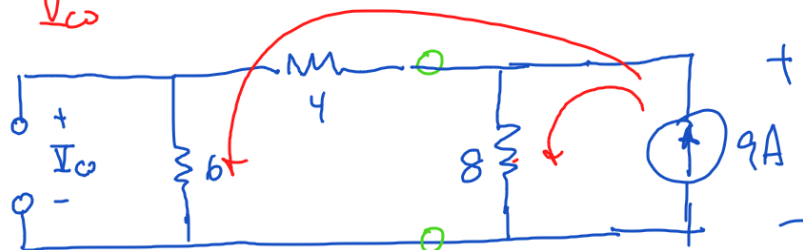


$$V_{co} = 72 \cdot \frac{6}{6+12}$$

$$= 72 \cdot \left(\frac{1}{3}\right)$$


$$V_{co} = 24V \quad \checkmark$$

V_{cap} continuous
 I_{ind} continuous

$$v_c(t=0^+) = 24V$$

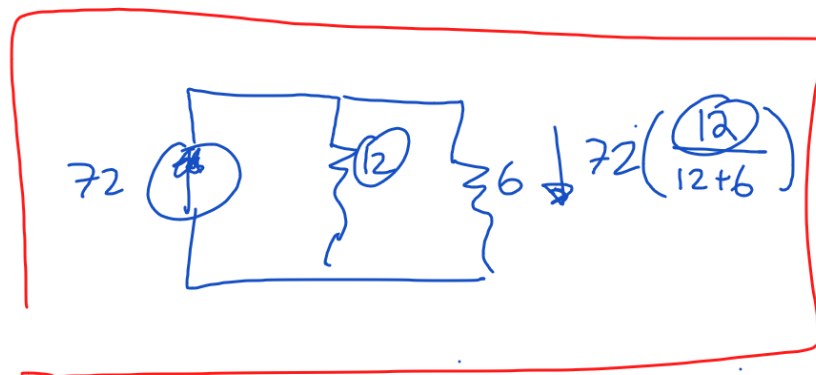

3)



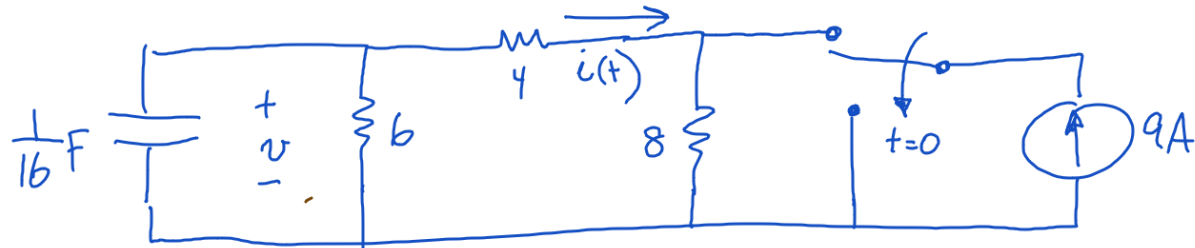


Voltage Dividers
Current Dividers

Problem 3/5

Find $v(t)$ and $i(t)$ for all time

② $t > 0$ Find τ

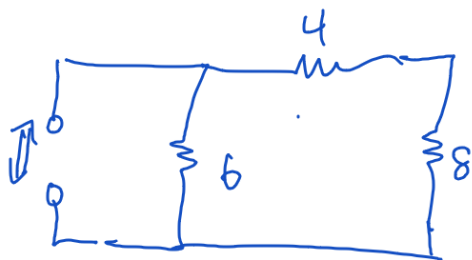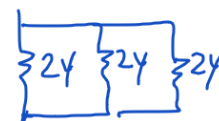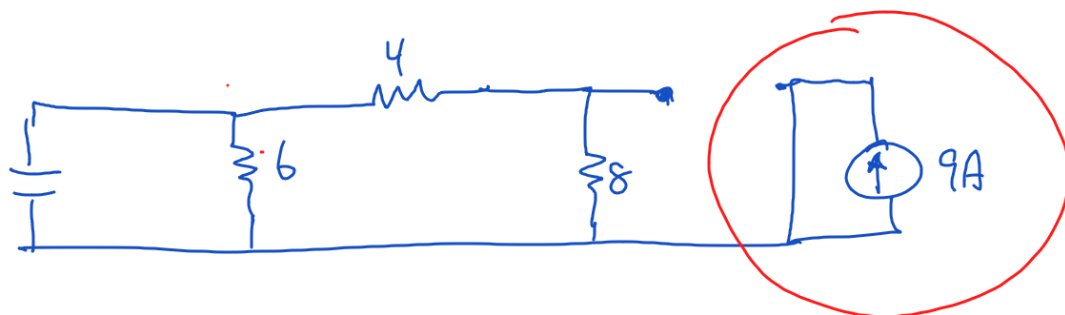

$$R_{eq} = 6 \parallel (4+8)$$

$$= 6 \parallel 12$$

$$= 4$$

~~$$\frac{1}{\frac{1}{6} + \frac{1}{12}}$$~~


$$\frac{6 \cdot 12}{6 + 12} \checkmark$$



$$\tau = R_{eq} \cdot C$$


$$= 4 \cdot \frac{1}{16}$$

$$= \boxed{\frac{1}{4} \text{ s}}$$

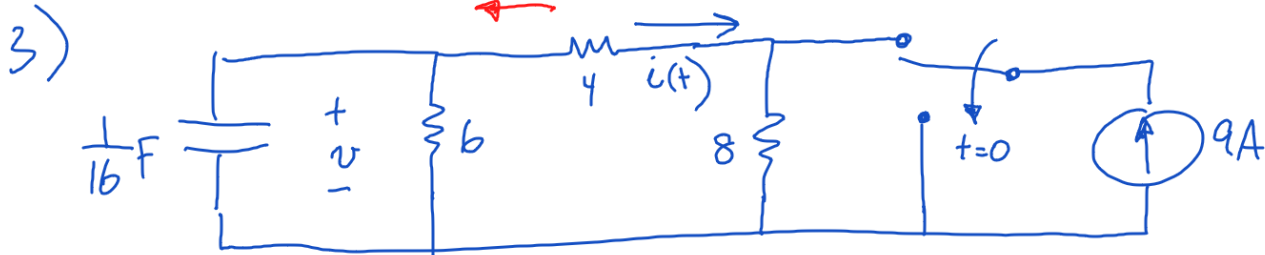

Find $v(t)$ and $i(t)$ for all time

③ $t = \infty$ $V_{c\infty}$

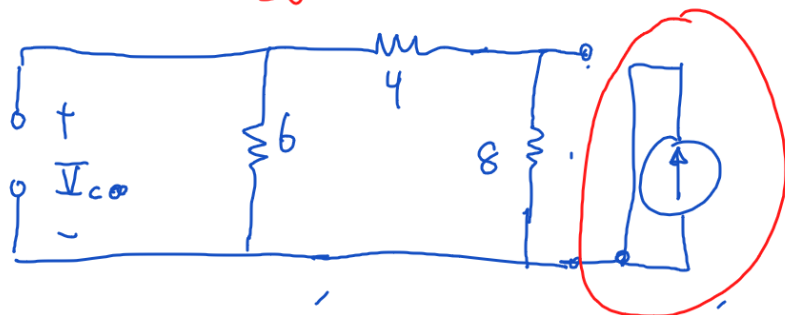

④ $0 \leq t < \infty$

$$v_c(t) = V_{\infty} + (V_0 - V_{\infty})e^{-\frac{t}{\tau}}$$

$$= 24e^{-4t}, t \geq 0$$



$$v_c(t) = \begin{cases} 24 & t < 0 \\ 24e^{-4t} V & t \geq 0 \end{cases}$$

⑤ Find asked to find

$$t < 0 \quad i = -4A$$

$$t > 0$$

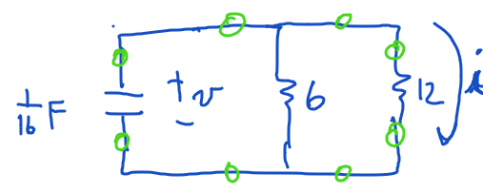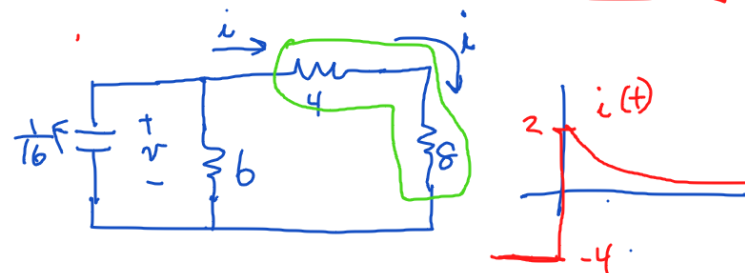
$$i(t) = \begin{cases} -4A & t < 0 \\ 2e^{-4t} A, t \geq 0 \end{cases}$$



$$i = \frac{v_2}{R_{12}}$$


$$= \frac{24e^{-4t}}{12}$$

$$= 2e^{-4t} A, t \geq 0$$

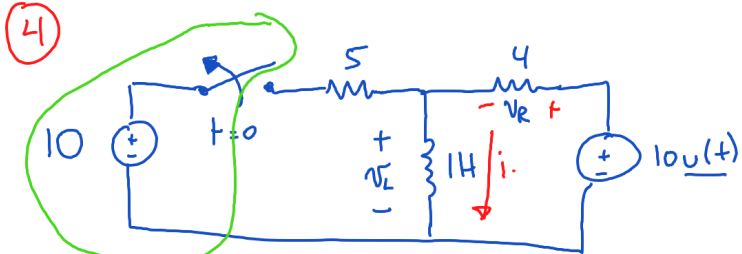


Find $v_L(t)$, $t \geq 0$

① $t < 0$ Find I_{L0}

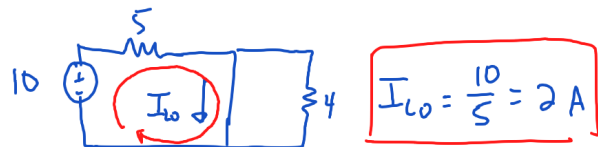


② $t > 0$ τ

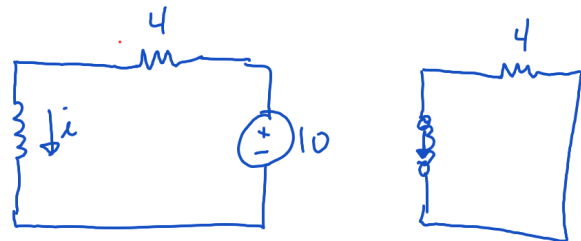

$$R_{eq} = 4\Omega \quad \tau = RC = \frac{L}{R} = \frac{1}{4}$$

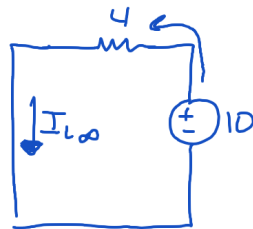③ $t = \infty \quad I_{L\infty} = \frac{10V}{4\Omega} = \frac{5}{2} A$




④ $i(t) = I_{\infty} + (I_0 - I_{\infty})e^{-t/\tau}$
 $= \frac{5}{2} - \frac{1}{2}e^{-4t} A, t \geq 0$

⑤ KVL: $+v_L - 10 + v_R = 0$

$$\begin{aligned} v_L &= 10 - v_R \\ &= 10 - i \cdot 4 \\ &= 10 - [10 - 2e^{-4t}] \\ &= 2e^{-4t} V \end{aligned}$$


— Different way —
 $v_L = L i'$
 $= (\frac{5}{2} - \frac{1}{2}e^{-4t})'$
 $= 2e^{-4t} V$ ★

5

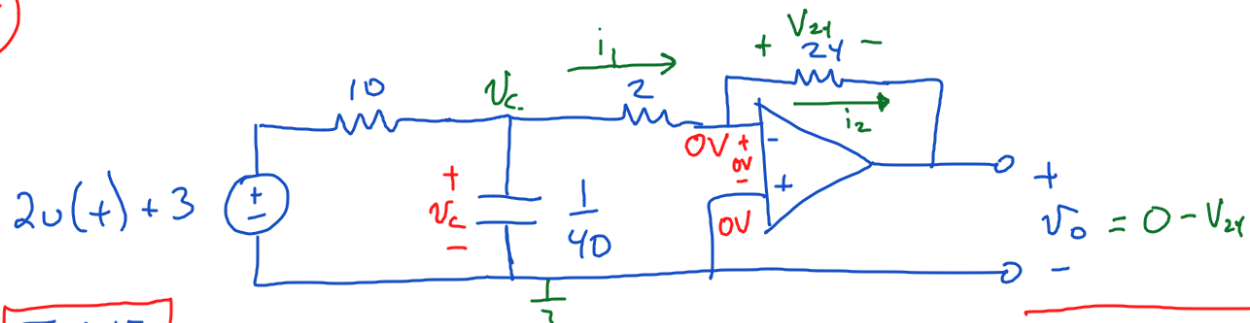

Find v_o

① $t < 0$

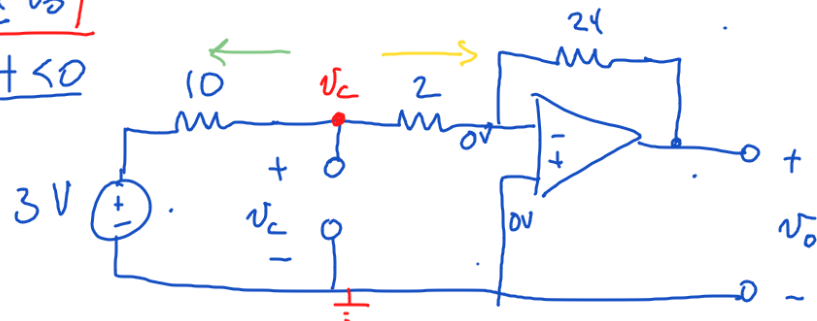


$$\frac{v_c - 3}{10} + \frac{v_c - 0}{2} = 0$$

$$v_c - 3 + 5v_c = 0$$

$$6v_c = 3 \Rightarrow v_o = \frac{1}{2}$$

② $t > 0$ τ

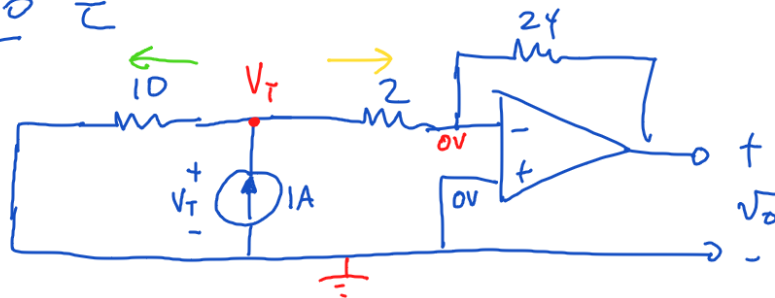

Zero all indep. sources

$$\frac{v_T - 0}{10} + \frac{v_T - 0}{2} + -1 = 0$$

$$v_T + 5v_T = 10$$

$$6v_T = 10$$

$$3v_T = 5$$

$$v_T = \frac{5}{3} V$$

$$R_{eq} = \frac{v_T}{I_T} = \frac{5/3}{1} = \frac{5}{3}$$

$$\tau = R_{eq}C = \left(\frac{5}{3}\right)\left(\frac{1}{40}\right) = \frac{1}{24} s$$


Golden Rules for Opamps

$$① i^+ = 0$$

$$i^- = 0$$

$$② \text{if neg feedback } v^+ = v^-$$

③ $t = \infty$

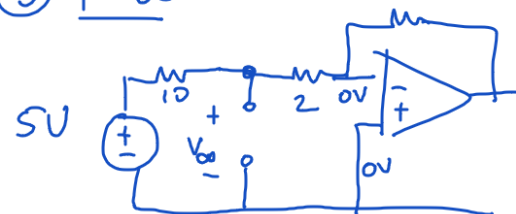

$$\frac{v_o - 5}{10} + \frac{v_o - 0}{2} = 0$$

$$v_o - 5 + 5v_o = 0$$

$$6v_o = 5 \Rightarrow v_o = \frac{5}{6}$$

$$④ v_c(t) = v_o + (v_o - v_o)e^{t/\tau}$$

$$= \frac{5}{6} - \frac{1}{3} e^{-24t} V, t \geq 0$$

⑤ $v_o = ?$

$$① i_1 = \frac{v_c - 0}{2} = \frac{v_c}{2}$$

$$② i_2 = i_1 = \frac{v_c}{2}$$

$$③ v_{24} = i_2 \cdot 24 = \frac{v_c}{2} \cdot 24 = 12v_c$$

$$④ v_o = -v_{24} = -12v_c$$

$$v_o = -10 + 4e^{-24t} V$$

$$\left. \begin{array}{l} 0 + v_{24} + v_o = 0 \\ v_o = -v_{24} \end{array} \right\}$$