
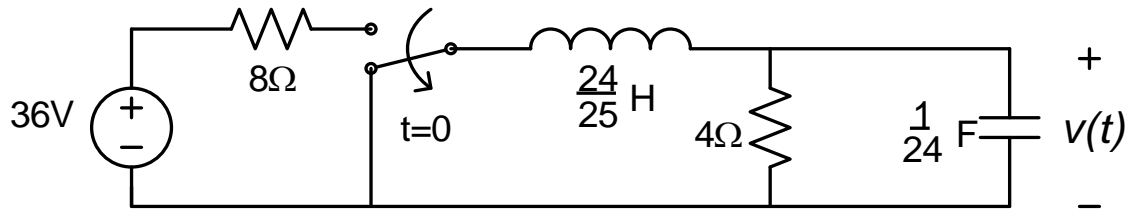


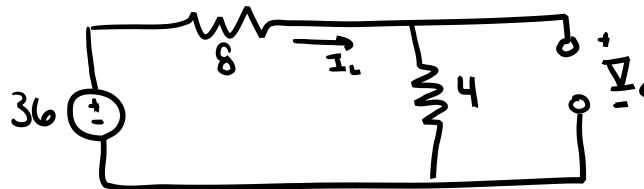1. Find the initial conditions $v(0^+)$, $v'(0^+)$.




$$v(0) \Rightarrow + < 0$$



$$I_c = \frac{36}{12} = 3A$$

$$V_c = 36 \frac{4}{4+8} = 12V$$

$$v'(0) \Rightarrow t=0^+$$

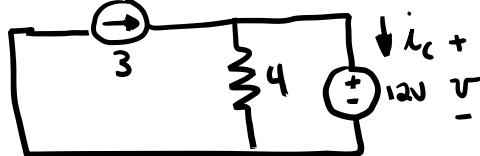

$$i_c = C v'$$

$$v'(0) = \frac{1}{C} i_c$$

$$= \frac{1}{C} (3 - 12/4)$$

$$= 0 \text{ V/s}$$

$$v(0) = 12V$$

$$v'(0) = 0 \text{ V/s}$$

2. Find $v_{nat}(t)$


$$v_{nat} \Rightarrow + > 0$$

$$\alpha = \frac{1}{2RC} = 3$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 5$$


$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -3 \pm j4$$

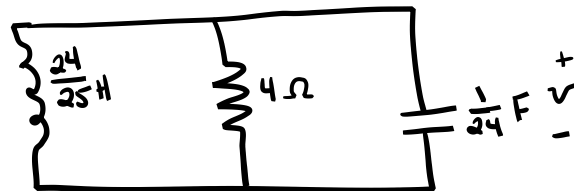



$$v_{nat}(t) = e^{-3t} [C_1 \cos 4t + C_2 \sin 4t]$$

3. Find $i(t)$ for $t \geq 0$.

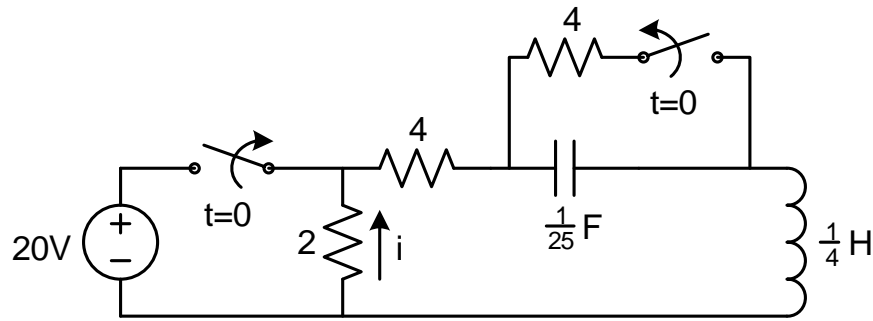


① Find IC

a) $t < 0$
Find V_C, i_L

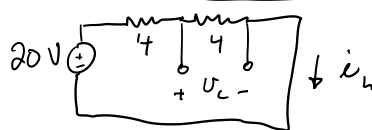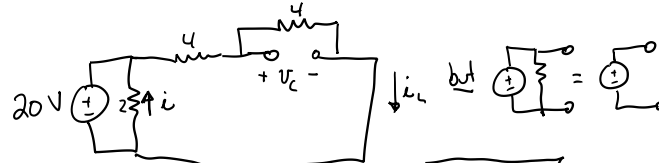

$$\begin{aligned} V_C &= 10V \text{ by } V_{\text{divider}} \quad 20 \left(\frac{4}{4+4} \right) \\ i_L &= 2.5A \text{ by } \Omega\text{'s Law } \frac{20}{8} \end{aligned}$$


b) $t = 0^+$
Find i, i'

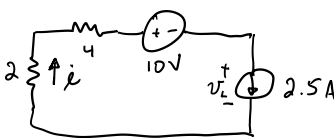

$$\begin{aligned} \text{by inspection } i &= 2.5A \\ V_L &= L i' \Rightarrow i' = \frac{1}{L} V_L \\ \text{by KVL, } 2(2.5) + 4(2.5) + 10 + V_L &= 0 \\ \Rightarrow V_L &= -25V \\ \text{so } i' &= \frac{1}{L} V_L = 4(-25) \\ i' &= -100 A/s \end{aligned}$$

② Find natural solution

a) $t > 0$

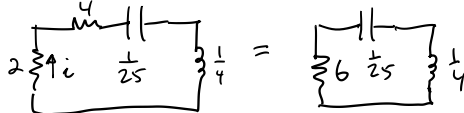

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{100}}} = 10$$

$$\alpha = \frac{R}{2L} = \frac{6 \cdot 4}{2} = 12$$

$$\begin{aligned} S &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ &= -18.6, -5.37 \end{aligned}$$

b) $\alpha > \omega_0 \Rightarrow$ overdamped

$$\Rightarrow i_n(t) = C_1 e^{-18.6t} + C_2 e^{-5.37t}$$

③ Find forced solution $t = \infty$ there are no sources $\Rightarrow i_f = 0$ by inspection

④ Find total response

$$\begin{aligned} \text{a) } i(t) &= C_1 e^{-18.6t} + C_2 e^{-5.37t} \Rightarrow i(0) = C_1 + C_2 = 2.5 \\ \text{b) } i'(t) &= -18.6 C_1 e^{-18.6t} - 5.37 C_2 e^{-5.37t} \Rightarrow i'(0) = -18.6 C_1 - 5.37 C_2 = -100 \end{aligned}$$

$$\begin{bmatrix} 1 & 1 \\ -18.6 & -5.37 \end{bmatrix} \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} 2.5 \\ -100 \end{bmatrix} \text{ by calc } \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} 6.53 \\ -4.03 \end{bmatrix}$$

$$\Rightarrow i(t) = 6.53 e^{-18.6t} - 4.03 e^{-5.37t} A$$