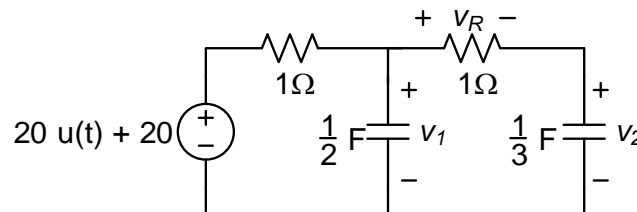


You have a large selection of collaborative problems, homework problems, and solved problems in your text already that are at the level of difficulty of the test. When you are ready for a challenge, here are three problems at a difficulty level slightly greater than that of the test.

P1 Concept: Initial Conditions


Find: $v_R(0^+)$ and $v_R'(0^+)$ in the following circuit

Hints: RCC initial conditions are solved the same way as LRC, except that instead of finding $v_C(0)$ and $i_L(0)$ first you'll find $v_{C1}(0)$ and $v_{C2}(0)$.



Find $v_R(0^+)$, $v_R'(0^+)$


$t < 0$

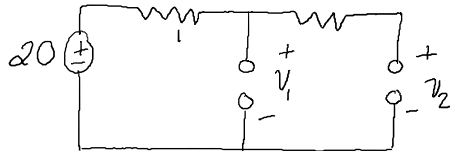

By inspection $v_1 = v_2 = 20V$

(No indicator, so find the IC's of the C's)

$t = 0$

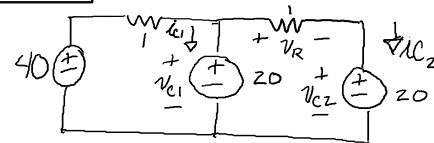

$$v_R = 20 - 20 = 0V$$

$$i_{C1} = C v_{C1}'$$

$$\Rightarrow v_{C1}' = \frac{1}{C_1} i_{C1} = (2)(20) = 40V/s$$

$$v_{C2} = \frac{1}{C_2} i_{C2} = (3)(0) = 0V/s$$

$$\text{KVL right Loop: } +v_R = -v_2 + v'$$

$$v_R = -v_2' + v'$$

$$= -0 + 40'$$

$$= 40V/s$$

$$\text{KCL top middle: } \frac{20-40}{1} + i_{C1} + \frac{20-20}{1} = 0$$

$$\Rightarrow i_{C1} = 20A$$

$$\text{KCL top Right: } \frac{20-20}{1} = i_{C2} = 0$$

$$\text{So } \boxed{v_R(0^+) = 0V}$$

$$\boxed{v_R'(0^+) = 40V/s}$$

- P2 Concept:** Find i (parallel) or v (series) of an RLC circuit
Find: Find $v_C(t)$ in the following RLC circuit for $t \geq 0$.
Hints: There are several 3's in the answer

①

Parallel, so $v_o = v_C = 3V$
 $v_o' = \frac{1}{C} i_C$
 KVC top: $\frac{3}{6} - \frac{1}{2} + i_C = 0$
 $\Rightarrow i_C = 0A$
 $\Rightarrow v_o' = \frac{1}{C} i_C = 0$

$i_{L0} = -\frac{6}{6+6}$ by Ω 's law $= -\frac{1}{2}A$
 $v_{C0} = (6V) \left(\frac{6\Omega}{6\Omega+6\Omega} \right) = 3V$ by voltage divider

② $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{9}} = \frac{1}{3}$
 $\alpha = \frac{1}{2RC} = \frac{1}{3}$ } Critically damped

③ $S = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\frac{1}{3}, -\frac{1}{3} \Rightarrow v_n(t) = C_1 e^{-\frac{1}{3}t} + C_2 t e^{-\frac{1}{3}t}$

④ $t = \infty$ no sources $\Rightarrow v_f = 0$

⑤ $v(t) = v_n(t) + v_f(t) = C_1 e^{-\frac{t}{3}} + C_2 t e^{-\frac{t}{3}}$ now match IC
 $v(0) = C_1 = 3$ so
 $v(t) = 3e^{-\frac{t}{3}} + C_2 t e^{-\frac{t}{3}}$
 $v'(t) = -e^{-\frac{t}{3}} + C_2 \left(-\frac{1}{3} \right) e^{-\frac{t}{3}} + C_2 e^{-\frac{t}{3}}$ by product rule
 $v'(0) = -1 + C_2(0) + C_2 \Rightarrow 0 = -1 + C_2 \Rightarrow C_2 = 1$
 $v(t) = 3e^{-\frac{t}{3}} + t e^{-\frac{t}{3}}$



⑥

$$v(t) = \begin{cases} 3, & t < 0 \\ (3+t)e^{-\frac{t}{3}}, & t \geq 0 \end{cases}$$

P3 Concept: Find any i or v in an RLC circuit

Find: Find $v_C(t)$ in the following RLC circuit for $t \geq 0$.

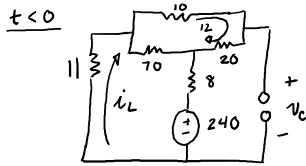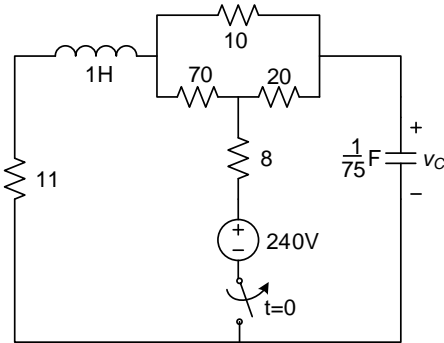Hints: One root of s is -5 , and there is a 117 in the answer



Mesh:

$$i_L: 11i_L + 70(i_L - i_2) + 8i_L + 240 = 0$$

$$\Rightarrow 89i_L - 70i_2 = -240$$

$$i_2: 10i_2 + 20i_2 + 70(i_2 - i_L) = 0$$


$$\Rightarrow -70i_L + 100i_2 = 0$$

KVL Right loop $\oint: -v_C + 20i_2 + 8i_2 + 240 = 0$

$$v_C = 20(-4.2) + 8(-6) + 240 = 108V$$

SO $i_L(0^+) = -6A$
 $v_C(0^+) = 108V$
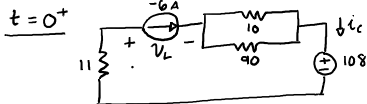
$$\begin{bmatrix} 89 & -70 \\ -70 & 100 \end{bmatrix} \begin{bmatrix} i_L \\ i_2 \end{bmatrix} = \begin{bmatrix} -240 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} i_L \\ i_2 \end{bmatrix} = \begin{bmatrix} -6 \\ -4.2 \end{bmatrix}$$




$$i_C = C v_C'$$

$$v_C(0^+) = 108V$$

$$v_C' = \frac{1}{C} i_C = \frac{1}{75}(-6) = -450 V/s$$

$$v_C'(0^+) = -450 V/s$$

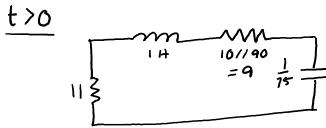

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1/75}} = \sqrt{75}$$

$$\alpha = \frac{R}{2L} = \frac{20}{2} = 10$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -10 \pm 5 = -5, -15$$

$$v_n(t) = C_1 e^{-5t} + C_2 e^{-15t}$$

$t = \infty$ No source $\Rightarrow v_C(\infty) = 0 \Rightarrow v_C = 0$

$$v(t) = v_n(t) + v_f(t) = C_1 e^{-5t} + C_2 e^{-15t}$$

$$\begin{cases} v(0) = C_1 + C_2 = 108 \\ v'(0) = -5C_1 - 15C_2 = -450 \end{cases} \Rightarrow \begin{bmatrix} 1 & 1 \\ -5 & -15 \end{bmatrix} \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} 108 \\ -450 \end{bmatrix} \Rightarrow \begin{bmatrix} C_1 \\ C_2 \end{bmatrix} = \begin{bmatrix} 117 \\ -9 \end{bmatrix}$$

$$v(t) = 117 e^{-5t} - 9 e^{-15t} V$$