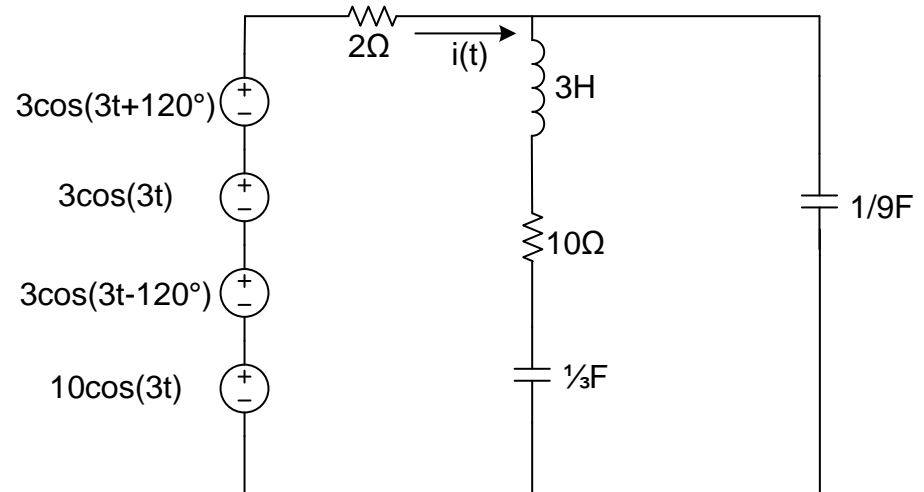


1. Simplify the following circuit to a single voltage source and impedance and solve for  $i(t)$ .



2. Find the current  $i(t)$ .

