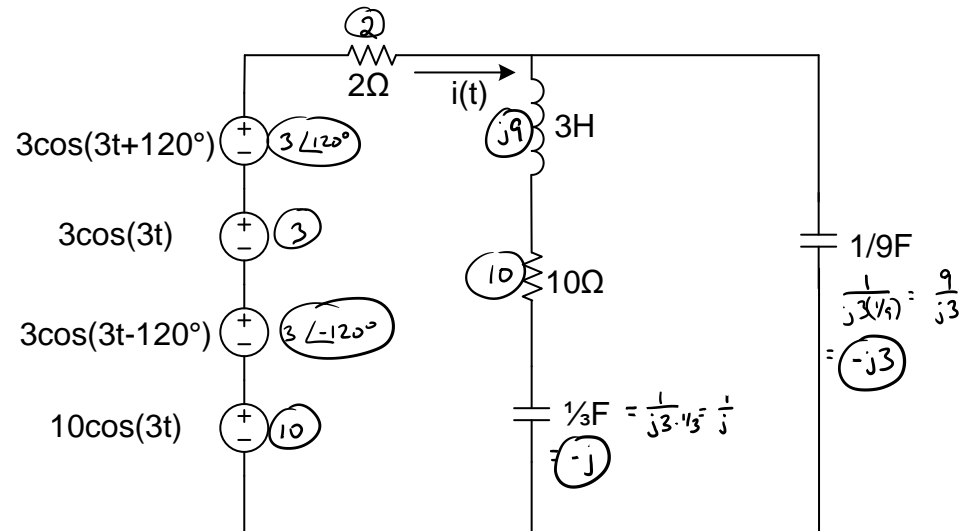


1. Simplify the following circuit to a single voltage source and impedance and solve for $i(t)$.



$$V_T = 3\angle 120^\circ + 3 + 3\angle -120^\circ + 10 = 10\angle 0^\circ$$

$$Z_T = 2 + [(j9 + 10 - j) \parallel -j3]$$

$$= 2 + (10 + j8) \parallel (-j3)$$

$$= 2 + \frac{(-j3)(10 + j8)}{10 + j8 - j3}$$


$$= 2 + \frac{(-j3)(10 + j8)}{10 + j5}$$

$$= 4.32\angle -51^\circ$$

$$I = \frac{V_T}{Z_T} = \frac{10\angle 0^\circ}{4.32\angle 51^\circ} = 2.31\angle 51^\circ$$



$$i(t) = 2.31 \cos(3t + 51^\circ) \text{ A}$$

2. Find the current $i(t)$.

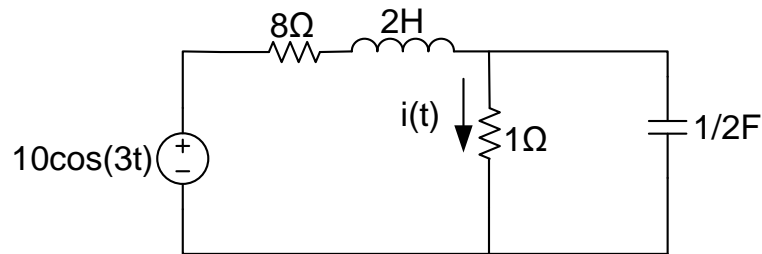

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(3)(1/2)} = -j\frac{2}{3}$$


$$Z_L = j\omega L = j3 \cdot 2 = j6$$

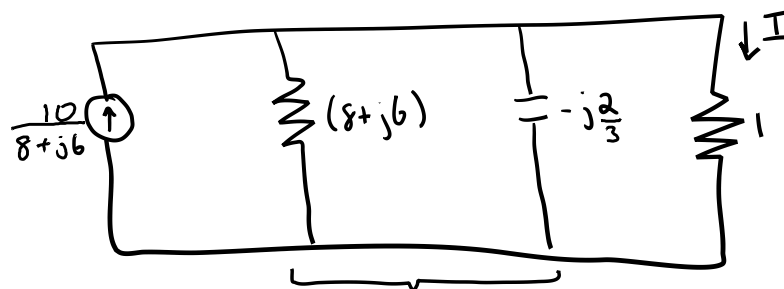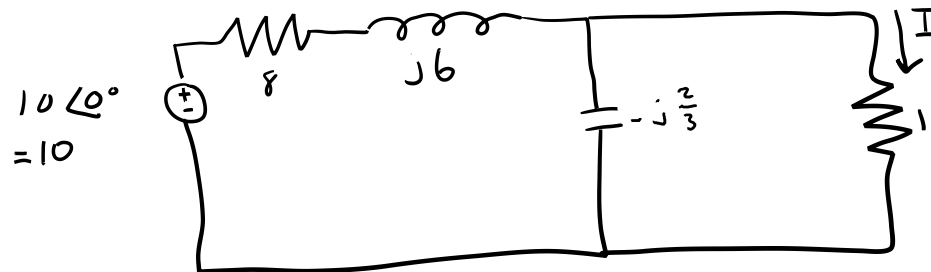

$$\frac{10}{8 + j6} = 1 \angle -36.9^\circ$$

$$Z_{eq} = (8 + j6) \parallel -j\frac{2}{3} = \frac{(8 + j6)(-j2/3)}{8 + j6 - j2/3} = 0.693 \angle -86.8^\circ$$

Z in parallel

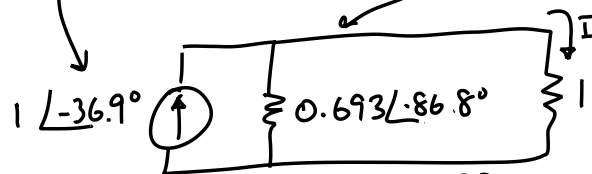

$$I = 1 \angle -36.9^\circ \left(\frac{0.693 \angle -86.8^\circ}{1 + 0.693 \angle -86.8^\circ} \right) \quad \text{Current divider}$$

$$= 0.556 \angle -90^\circ$$

$$\boxed{i(t) = 0.556 \cos(3t - 90^\circ) \text{ A}} \quad \text{or to show off, } i = 0.556 \sin(3t) \text{ A}$$