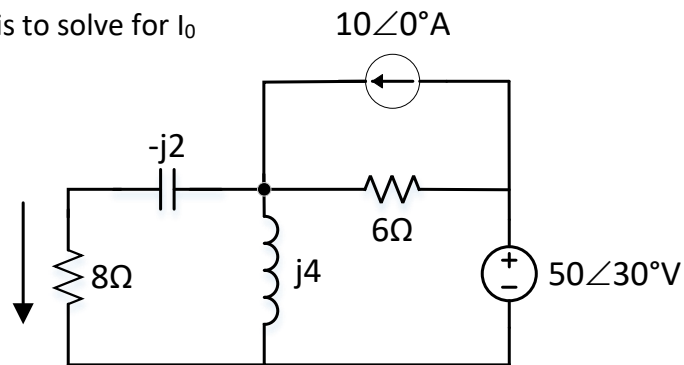


1. Use mesh analysis to solve for I_0



2. Challenging!

Find I_0 in the circuit below. Will need a supermesh.

Hint: where will the supermesh go? Write it in terms of I_1 .

