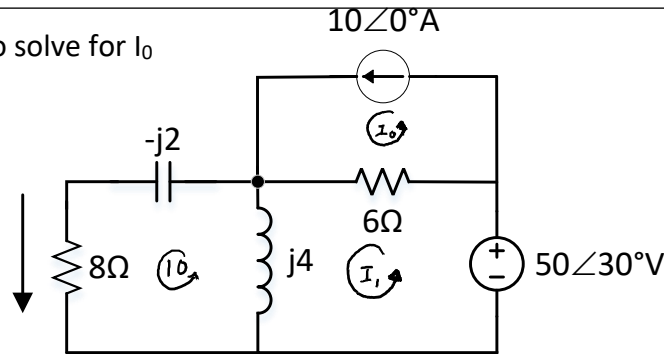


1. Use mesh analysis to solve for  $I_0$



$$\text{KVL } I_0: -j2 I_0 + 8 I_0 + j4(I_0 - I_1) = 0 \Rightarrow I_0(8 + j2) + I_1(-j4) = 0$$


$$\text{KVL } I_1: -50\angle 30^\circ + 6(I_1 - I_0) + j4(I_1 - I_0) = 0 \Rightarrow I_0(-j4) + I_1(6 + j4) = 60 + 50\angle 30^\circ = 103.3 + j25$$

$$\begin{bmatrix} 8+j2 & -j4 \\ -j4 & 6+j4 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \end{bmatrix} = \begin{bmatrix} 0 \\ 103.3 + j25 \end{bmatrix} \Rightarrow \begin{bmatrix} I_0 \\ I_1 \end{bmatrix} = \begin{bmatrix} 5.97\angle 65.4^\circ \\ 12.3\angle -10.5^\circ \end{bmatrix} \Rightarrow \boxed{I_0 = 5.97\angle 65.4^\circ \text{ A}}$$

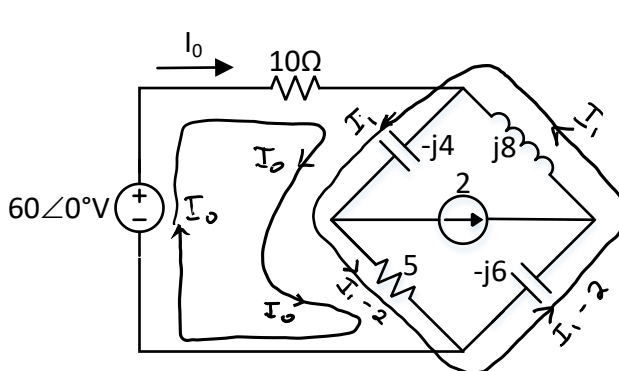2. Challenging!

Find  $I_0$  in the circuit below. Will need a supermesh.

Hint: where will the supermesh go? Write it in terms of  $I_1$ .



Left loop (starting left)

$$-60 + 10I_0 + (I_0 + I_1)(-j4) + (I_0 + I_1 - 2)5 = 0$$

$$I_0(10 - j4 + 5) + I_1(-j4 + 5) = 60 + 10$$

Diamond loop (starting at right)

$$I_1 j8 + (I_0 + I_1)(-j4) + (I_0 + I_1 - 2)5 + (I_1 - 2)(-j6) = 0$$

$$I_0(-j4 + 5) + I_1(j8 - j4 + 5 - j6) = 10 - j12$$

$$\begin{bmatrix} 15-j4 & 5-j4 \\ 5-j4 & 5-j2 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \end{bmatrix} = \begin{bmatrix} 70 \\ 10-j12 \end{bmatrix} \Rightarrow \begin{bmatrix} I_0 \\ I_1 \end{bmatrix} = \begin{bmatrix} 5.95\angle 3.2^\circ \\ 4.34\angle 176^\circ \end{bmatrix}$$

$$\Rightarrow \boxed{I_0 = 5.95\angle 3.2^\circ \text{ A}}$$