
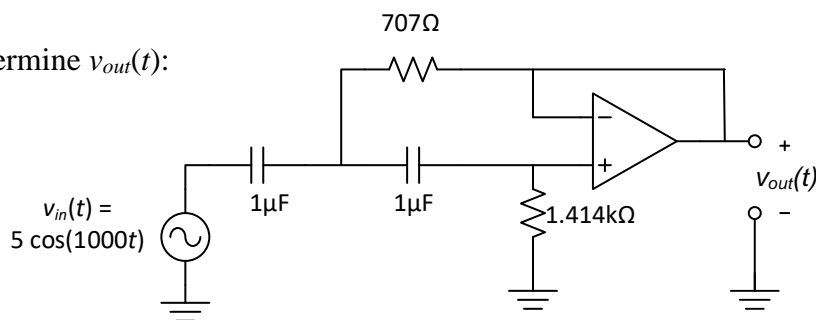


P1 Determine  $v_{out}(t)$ :

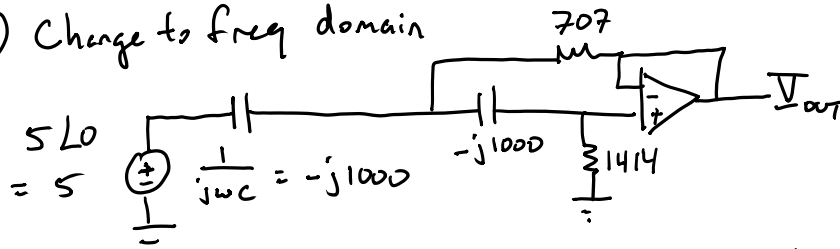


Hint: Answer's phase should be close to  $90^\circ$ .

① Change to freq domain



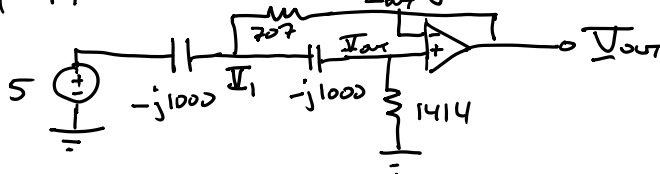② Opamp, so use Nodal, noting  $V^+ = V^-$  so only 1 variable there



③ Opemamp, so do not do a KCL @ output

$$I_1: \frac{V_1 - 5}{-j1000} + \frac{V_1 - V_{out}}{-j1000} + \frac{V_1 - V_{out}}{707} = 0 \quad \left| \begin{array}{l} \text{group variables on left,} \\ \text{constants on right} \end{array} \right.$$

$$I_2: \frac{V_{out} - V_1}{-j1000} + \frac{V_{out}}{1414} = 0$$

$$I_1: \left( \frac{1}{-j1000} + \frac{1}{-j1000} + \frac{1}{707} \right) V_1 + V_{out} \left( \frac{1}{j1000} - \frac{1}{707} \right) = -\frac{5}{j1000} \quad \left| \begin{array}{l} \text{put in a matrix} \end{array} \right.$$

$$I_2: \left( \frac{1}{j1000} \right) V_1 + V_{out} \left( \frac{1}{-j1000} + \frac{1}{1414} \right) = 0$$

$$\begin{bmatrix} 0.00141 + j0.002 & -0.00141 - j0.001 \\ -j0.001 & 0.000707 + j0.001 \end{bmatrix} \begin{bmatrix} V_1 \\ V_{out} \end{bmatrix} = \begin{bmatrix} j0.005 \\ 0 \end{bmatrix} \quad \text{calc in polar, degrees}$$


$$\Rightarrow \begin{bmatrix} V_1 \\ V_{out} \end{bmatrix} = \begin{bmatrix} 4.33 \angle 54.7^\circ \\ 3.54 \angle 90^\circ \end{bmatrix}$$

④ Convert to time domain:  $v_{out}(t) = 3.54 \cos(1000t + 90^\circ) \text{ V}$

**P2** What is  $V_{out}(t)$  if we change  $v_{in}(t)$  to 5V (i.e. a DC signal of  $\omega = 0$  rad/s)

Here  $\omega = 0$  so  $Z_c = \frac{1}{j\omega C} = \infty = \text{an open}$

① Redraw in freq domain 707

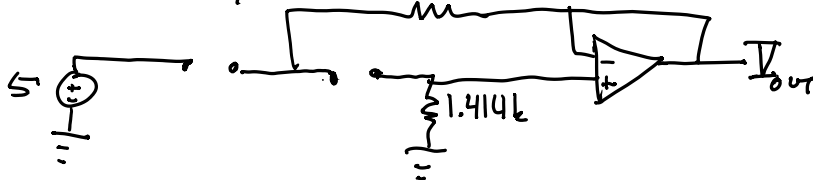

Could redo phasor analysis, but smarter to use intuition


a)  $V^+ = 0$  by sight ( $I = 0$  so no voltage drop across  $R$ )

b)  $V^- = V^+ = 0$  since opamp

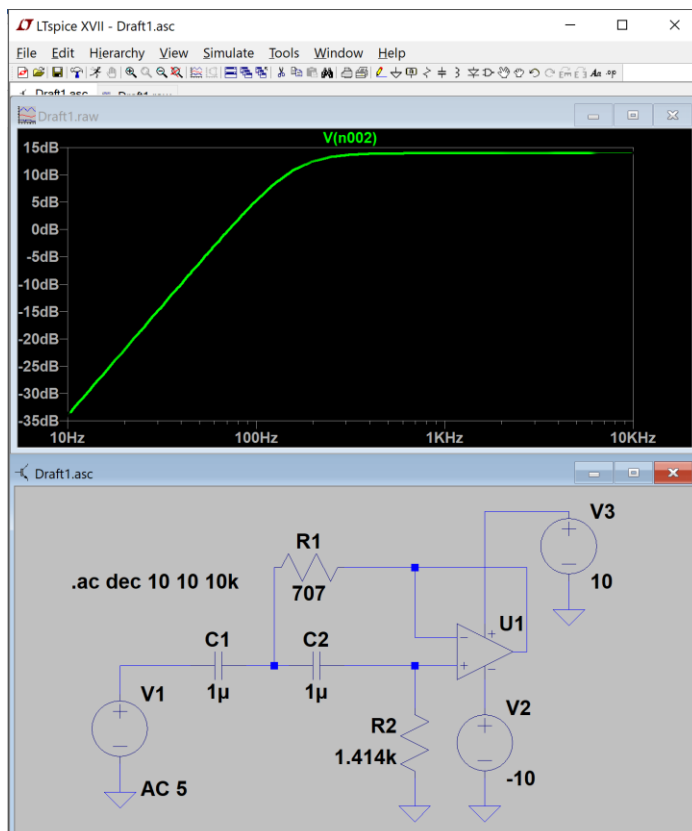c)  $V_{out} = V^- = 0$  since connected by a wire

②  $V_{out}(t) = 5V$

**P3** Plot the magnitude of  $v_{out}(t)$  as the input frequency changes from 10 to 10kHz using LTspice. This is an example of a *filter*. Does it pass low or high frequencies?



Use UniversalOpamp2  
Passes high frequencies