



If $v(t) = 155.6 \cos(2\pi 60t + 85^\circ) V$
and $i(t) = 565.7 \cos(2\pi 60t + 15^\circ) mA$

Find

- V_{RMS} and I_{RMS} phasors.
- Complex power phasor (include units). Draw power triangle.
- Apparent power (include units).
- Real power (include units).
- Reactive power (include units).
- Power factor (include leading or lagging).
- Load impedance in Ω .
- Model of load impedance as series RL or RC.
- Average power dissipated in load (include units).