

If $v(t) = 155.6 \cos(2\pi 60t + 85^\circ) V$
 and $i(t) = 565.7 \cos(2\pi 60t + 15^\circ) mA$

Find


- a) V_{RMS} and I_{RMS} phasors.

$$\underline{V}_{RMS} = \frac{155.6}{\sqrt{2}} \angle 85^\circ V_{RMS} = \boxed{110 \angle 85^\circ V_{RMS}}$$

$$\underline{I}_{RMS} = \frac{565.7}{\sqrt{2}} \angle 15^\circ A_{RMS} = \boxed{400 \angle 15^\circ mA_{RMS}}$$

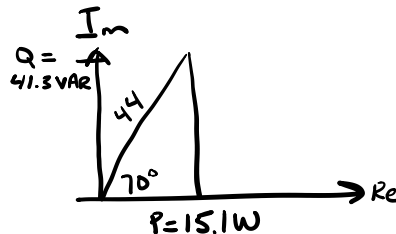- b) Complex power phasor (include units). Draw power triangle.

$$\underline{S} = \underline{V}_{RMS} \underline{I}_{RMS}^* = (110 \angle 85^\circ)(0.4 \angle -15^\circ) = \boxed{44 \angle 70^\circ VA} \text{ OR } \boxed{15.1 + j41.3 VA}$$



- c) Apparent power (include units).

$$S = |\underline{S}| = \boxed{44 VA}$$

- d) Real power (include units).

$$P = \text{Re} \{ \underline{S} \} = 44 \cos(70^\circ) = \boxed{15.1 W} \text{ (or, from triangle above)}$$

- e) Reactive power (include units).

$$Q = \text{Im} \{ \underline{S} \} = 44 \sin(70^\circ) = \boxed{41.3 VAR} \text{ (or, from triangle above)}$$

- f) Power factor (include leading or lagging).

$$pf = \cos(70^\circ) = \boxed{0.342 \text{ lagging}} \text{ since } \theta_I = 15^\circ < \theta_V = 85^\circ$$

g) Load impedance in Ω .

$$Z_{LOAD} = \frac{V_{LOAD}}{I_{LOAD}} = \frac{155.6 \angle 85^\circ}{565.7 \angle 15^\circ} = \boxed{94 + j258 \Omega}$$

h) Model of load impedance as series RL or RC.

$$R = 94 \Omega$$

$$L : j\omega L = j2\pi 60 L = j258 \Rightarrow L = \frac{258}{2\pi 60} = 0.684$$



i) Average power dissipated in load (include units)

$$P_{ave} = P = \boxed{1501W} \text{ from part d}$$