

Find the value of the parallel capacitance needed to correct a load of 140kVAR at 0.85 lagging pf to unity pf. Assume load is supplied by 110V_{RMS} at 60Hz.