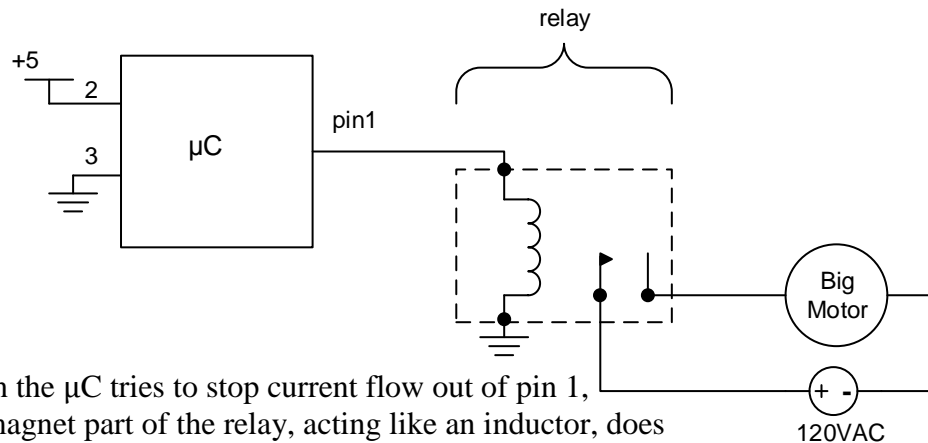


1. A relay is a momentary switch activated by an electromagnet (i.e., an inductor) allowing a small current low voltage source (like a microcontroller) to control heavy-duty sources (like an AC muter). In the circuit below, a microcontroller (abbrev. μC) turns on a relay by making pin 1 = 5V at $t=0$ sec. At $t=1$ sec it turns the relay off by trying to stop current flow out of pin 1 (internally disconnecting it).



At $t=1$ when the μC tries to stop current flow out of pin 1, the electromagnet part of the relay, acting like an inductor, does

- Nothing
- Tries to make the voltage at pin large and positive
- Tries to make the voltage at pin large and negative
- Tries to make the voltage at pin large and equal to zero

2. Could the action described in the preceding paragraph damage the μC ? If so, how could you use a diode to help? A diode, $\text{—}\blacktriangleright\text{—}$, is a device that only allows current to flow in the direction of the arrow (i.e. it looks like a short to current flowing in the direction of the arrow, but an open current flowing in reverse).